

# Verilog Tutorial

TA: 陳炫均


# Outline

- Introduction
- Major Data Types
- Operations
- Behavior Modeling
- Structure Modeling

# Outline

- Introduction
- Major Data Types
- Operations
- Behavior Modeling
- Structure Modeling

# IC Design Flow

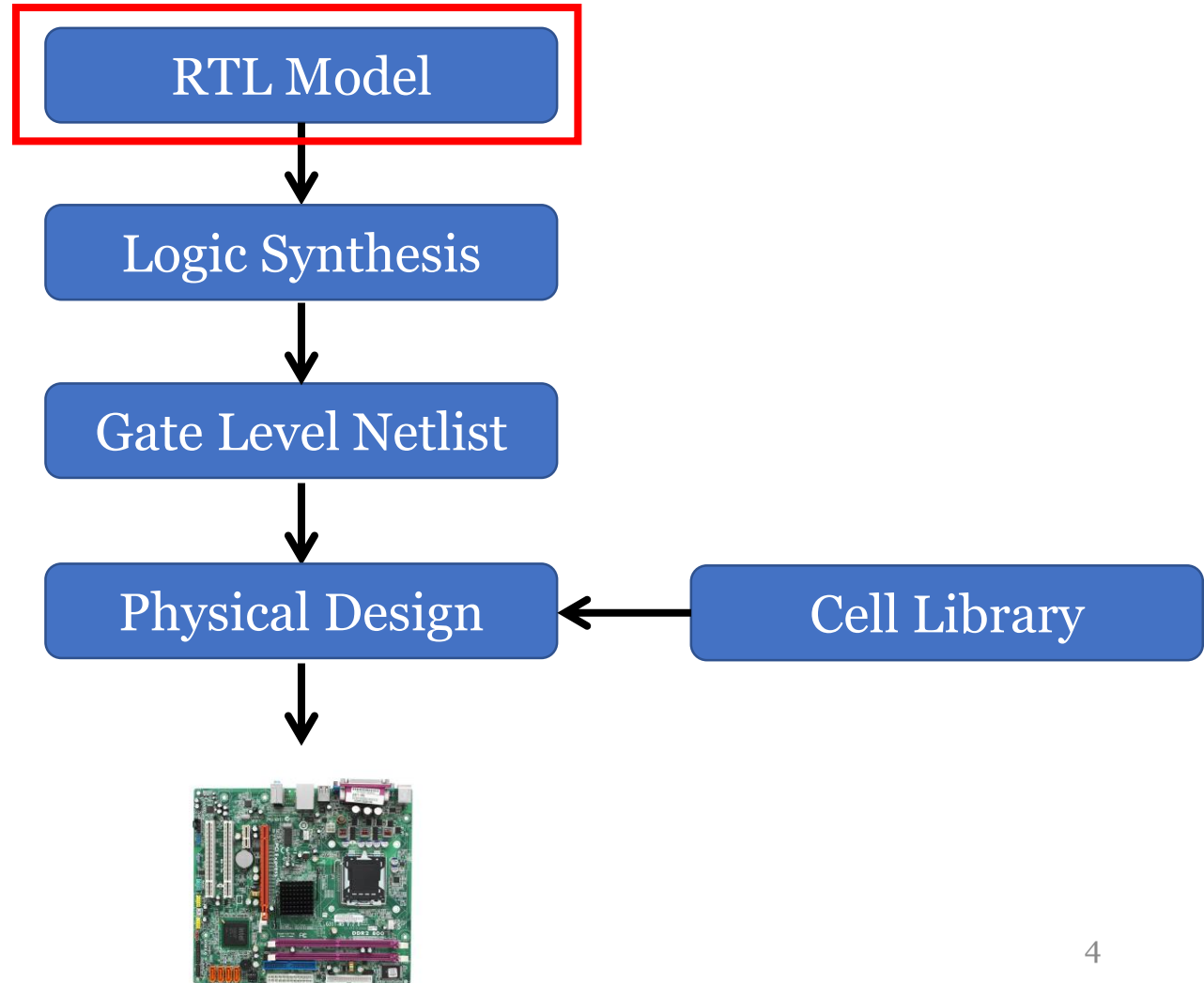

# Full Adder as an Example



```
module module_name (port_name);
```

Port Declaration

Data Type Declaration

Task & Function Declaration

Module Functionality or Structure

Timing Specification

```
endmodule
```

# Full Adder Example 1



module\_name


port\_name

```
1 module Full_Adder(sum, cout, a, b, ci);
2
3 //Interface
4 input      [31:0] a, b;
5 input      ci;
6 output     [31:0] sum;
7 output     cout;
8
9 wire       [32:0] tmp;
10
11 // Calculation (with continuous assignment)
12 assign tmp = a + b + ci;
13 assign sum = tmp[31:0];
14 assign cout = tmp[32];
15
16 endmodule
```

port declaration

data type declaration


module functionality

 
 
# Full Adder Example 2




```
1 module Full_Adder(sum, cout, a, b, ci);
2
3 //Interface
4 input      [31:0] a, b;
5 input      ci;
6 output     [31:0] sum;
7 output     cout;
8
9 // Calculation (with continuous assignment)
10 assign {cout, sum} = a + b + ci;
11
12 endmodule
```


 
# Full Adder Example 3



```
1 module Full_Adder(sum, cout, a, b, ci);
2
3 //Interface
4 input      [31:0] a, b;
5 input      ci;
6 output     [31:0] sum;
7 output     cout;
8
9 reg        [32:0] tmp;
10 // Calculation (with Always Procedural Block)
11 assign sum = tmp[31:0];
12 assign cout = tmp[32];
13
14 always@ (a or b or ci) begin
15     tmp = a + b + ci;
16 end
17
18 endmodule
```





# Port declaration

- declare input and output ports
  - input a;
  - output b;

```
module module_name (port_name);
```

Port Declaration

Data Type Declaration

Task & Function Declaration

Module Functionality or Structure

Timing Specification

```
endmodule
```

# Data Type Declaration

- Declare the data types used in the module
  - `wire [32:0] tmp;`
  - `reg [32:0] tmp;`

```
module module_name (port_name);
```

Port Declaration

**Data Type Declaration**

Task & Function Declaration

Module Functionality or Structure

Timing Specification

```
endmodule
```

# Task & Function Declaration

- Declare the modules used

```
alu ALU_instance(  
    .src_a(src_a),  
    .src_b(src_b),  
    .c(c), .data_out(data_out));
```

```
module module_name (port_name);
```

Port Declaration

Data Type Declaration

**Task & Function Declaration**

Module Functionality or Structure

Timing Specification

```
endmodule
```

# Module Functionality

- Describe the module behavior
  - `assign {cout, sum} = a + b + ci;`
  - `tmp = a + b + ci;`

```
module module_name (port_name);
```

Port Declaration

Data Type Declaration

Task & Function Declaration

**Module Functionality or Structure**

Timing Specification

```
endmodule
```

# Timing Specification

- Specify the time elapsed
  - #50;

```
module module_name (port_name);
```

Port Declaration

Data Type Declaration

Task & Function Declaration

Module Functionality or Structure

Timing Specification

```
endmodule
```

```
10 initial begin
11
12     $dumpfile("simpleALU.vcd");
13     $dumpvars;
14
15     src_a = 8'h55; // Time = 0
16     src_b = 8'h1a;
17     c = 3'b000;
18     #50; // Time = 50
19     c = 3'b001;
20     #50; // Time = 100
21     c = 3'b010;
22     #50; // Time = 150
23     c = 3'b011;
24     #50; // Time = 200
25     c = 3'b100;
26     #50; // Time = 250
27     c = 3'b101;
28     #50; // Time = 300
29     c = 3'b110;
30     #50; // Time = 350
31     c = 3'b111;
32 end
```

# Compiler Directives

- ``define`
  - ``define CYTLE_TIME 50`
  - Defining a name and gives a constant value to it
  - Like `#define CYCLE_TIME 50` in C
- ``include`
  - ``include adder.v`
  - Including the entire contents of other Verilog source file
  - Like `#include "adder.h"` in C
- ``timescale`
  - ``timescale 100ns/1ns`
  - Setting the reference time unit and time precision of the simulation

# System Tasks

- **\$monitor**

- `$monitor ($time, “%d %d %d”, a, b, cin);`
- Displays the values of the argument list whenever any of the arguments change except \$time

- **\$display**

- `$display (“%d %d %d”, a, b, cin);`
- Prints out the current values of the signals in the argument list
- Like “printf” in C

- **\$finish**

- `$finish;`
- Terminate the simulation

# Outline

- Introduction
- **Major Data Types**
- Operations
- Behavior Modeling
- Structure Modeling




# Major Data Types

- Wire (Net)
- Register
- Parameter
- Numbers

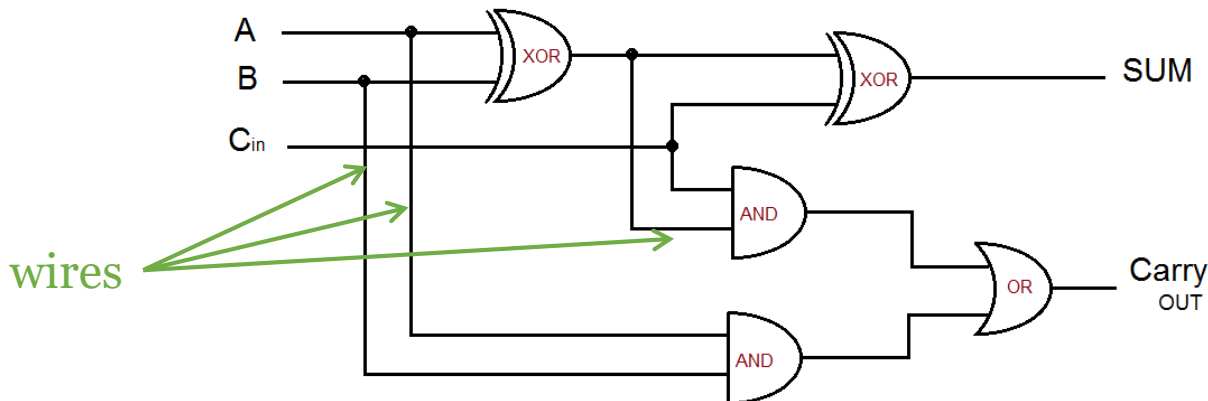
# Wire (Net)

- **Wires** represent physical connections between structural entities
- A **wire** must be driven by a driver, such as a gate or a **continuous assignment**.
- Verilog automatically propagates new values onto a wire when drivers change value.


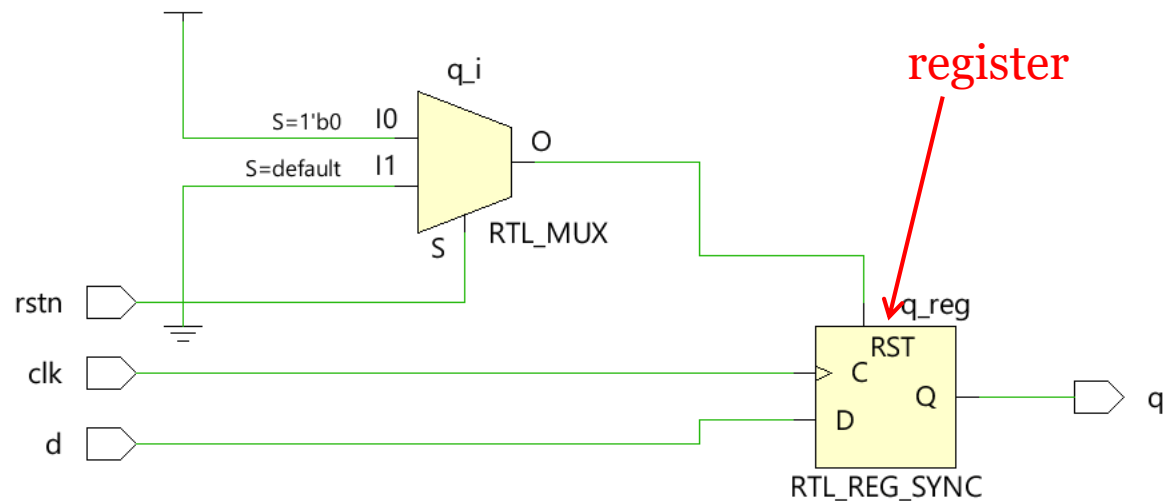
# Register

- Registers represent abstract storage elements
- A register holds its value until a new value is assigned to it
- Registers are used extensively in **behavior modeling**



# Assignment

- Continuous assignment
  - e.g. `assign c = a + b;`
  - the wire c will continuously be updated to value of a+b no matter what
- Procedural assignment
  - e.g. `c = 1;`
  - only executed when under some condition

# Parameter

- **Parameters** are not variables, they are **constants**.
- Typically parameters are used to specify delays and width of variables.

```
module var_mux(out, i0, i1, sel);  
  
    parameter width=2, delay=1;  
    output [width-1:0] out;  
    input  [width-1:0] i0, i1;  
    input                      sel;  
  
    assign #delay out = sel? i1 : i0;  
  
endmodule
```

# Wire and Registers

- Wire
  - Doesn't store value, just a connection
  - Cannot appear in “always” block assignment
  - input, output are default “wire”
  - Default value is Z (high-impedance)
- Register
  - A storage element
  - Assignment in “always” block
  - Event-driven modeling
  - Default value is X (unknown)

# Number Representation

- Format: `<size>'<base_format><number>`
- `<size>` - # of bits
  - Default is unsized and machine-dependent (but at least 32 bits)
- `<base_format>` - arithmetic base of *number*
  - `<d>` `<D>` - decimal, which is default base if *base\_format* is not given
  - `<h>` `<H>` - hexadecimal
  - `<o>` `<O>` - octal
  - `<b>` `<B>` - binary
- `<number>` - the value in base of *base\_format*
  - `_` can be inserted in between for readability

# Number Examples

Number	Binary value
6'b010_111	010111
8'b0110	00000110
4'bx01	xx01
16'H3AB	0000001110101011
24	000...00011000
5'O36	11110
16'Hx	xxxxxxxxxxxxxxxxxx
8'hz	zzzzzzzz
8'd16	00010000



# Outline

- Introduction
- Major Data Types
- **Operations**
- Behavior Modeling
- Structure Modeling


# Operators

Operator	Name
[ ]	bit-select or part-select
( )	parenthesis
!, ~	logical and bit-wise NOT
&,  , ~&, ~ , ^, ~^, ^~	reduction AND, OR, NAND, NOR, XOR, XNOR; If X=3'B 101 and Y=3'B 110, then X&Y=3'B 100, X^Y=3'B 011;
+, -	unary (sign) plus, minus; +17, -7
{ }	concatenation; {3'B 101, 3'B 110} = 6'B 101110;
{ { } }	replication; {3{3'B 110}} = 9'B 110110110
*, /, %	multiply, divide, modulus; <u>/ and % not be supported for synthesis</u>
+, -	binary add, subtract.
<<, >>	shift left, shift right; X<<2 is multiply by 4
<, <=, >, >=	comparisons. Reg and wire variables are taken as positive numbers.
=, !=	logical equality, logical inequality
==, !=	case equality, case inequality; <u>not synthesizable</u>
&	bit-wise AND; AND together all the bits in a word
^, ~^, ^~	bit-wise XOR, bit-wise XNOR
	bit-wise OR; AND together all the bits in a word
&&,	logical AND. Treat all variables as False (zero) or True (nonzero). logical OR. (7  0) is (T  F) = 1, (2  3) is (T  T) = 1, (3&&0) is (T&&F) = 0.
? :	conditional. x=(cond)? T : F;

**Table 5.1: Verilog Operators Precedence**

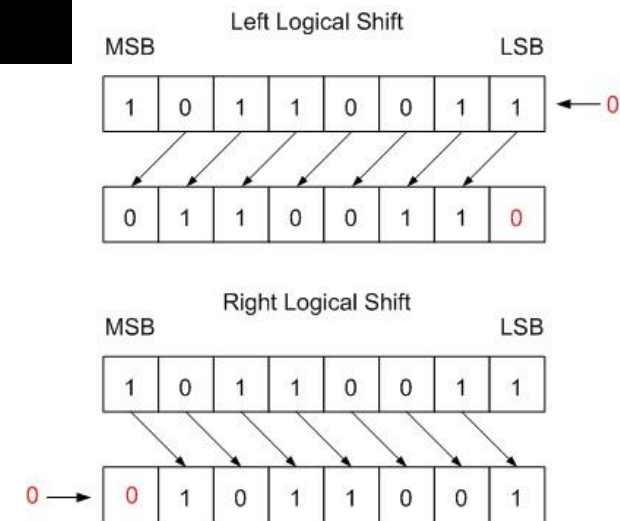
# Shift operator (logically)

```
1 module shift_register(reg_out, reg_in);
2
3 output [5:0] reg_out;
4 input  [5:0] reg_in;
5
6 parameter shift = 3;
7
8 assign reg_out = reg_in << shift;
9
10 endmodule
```



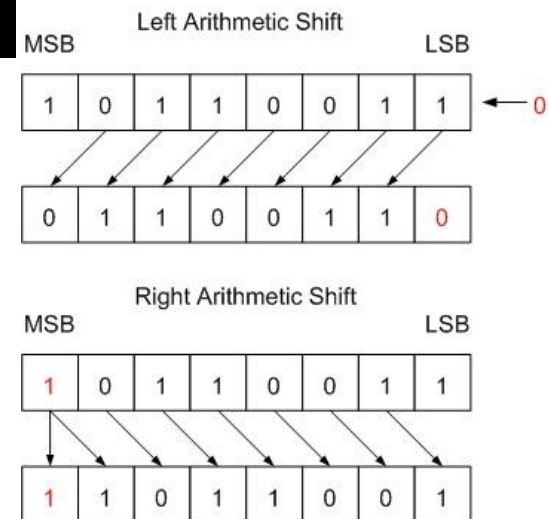
# Shift operator (arithmetically)

```
1 module shift_register(reg_out, reg_in);
2
3 output [5:0] reg_out;
4 input [5:0] reg_in;
5
6 parameter shift = 3;
7
8 assign reg_out = reg_in <<< shift;
9
10 endmodule
```



 
# Conditional operator

```
1 module MUX32(data1_i, data2_i, select_i, data_o);  
2 input  [31:0] data1_i, data2_i;  
3 input          select_i;  
4 output [31:0] data_o;  
5  
6 assign data_o = select_i? data2_i : data1_i;  
7  
8 endmodule
```


 
# Conditional operator (cont.)

```
1 module MUX4(out, i0, i1, i2, i3, sel);
2
3 output [3:0] out;
4 input [3:0] i0, i1, i2, i3;
5 input [1:0] sel;
6
7 assign out = (sel == 2'b00)? i0:
8              (sel == 2'b01)? i1:
9              (sel == 2'b10)? i2:
10             (sel == 2'b11)? i3:
11             4'bx;
12 endmodule
```



# Concatenation & Replication Operator

- Concatenation operator in LHS
  - `assign {co, sum} = a + b + c;`
- Bit replication to produce 01010101
  - `assign byte = {4{2'b01}};`

# Outline

- Introduction
- Major Data Types
- Operations
- **Behavior Modeling**
- Structure Modeling



# Behavior Modeling

- In behavior modeling, you must describe your circuits'
  - Action
    - How your circuits behave?
  - Timing control
    - At what time doing what thing
    - Under what condition do what thing
- Verilog supports followings to model circuits' behavior
  - Procedural block
  - Procedural assignment
  - Timing control
  - Control statement

# Procedural Blocks

- In Verilog, procedural blocks are the basic of behavior modeling
  - You can describe one behavior in one procedural block
- Procedural blocks are of two types
  - “**initial**” procedural block
    - execute only once
  - “**always**” procedural block
    - execute in a loop

# Procedural Blocks (cont.)

- All procedural blocks are activated at simulation time 0
- With **enabling condition**, the block will not be executed until the **enabling condition** is evaluated to TRUE
- Without **enabling condition**, the block will be executed immediately

# initial Block

```
10 initial begin
11
12     $dumpfile("Full_Adder.vcd");
13     $dumpvars;
14
15     // Time = 0
16     a  = 1'b0;
17     b  = 1'b0;
18     ci = 1'b0;
19
20 end
```

```
35 initial #1000
36     $finish;
```


# always Block

```
21 always@(posedge clk_i or posedge rst_i) begin
22     if(rst_i) begin
23         pc_o <= 32'b0;
24     end
25     else begin
26         if(start_i)
27             pc_o <= pc_i;
28         else
29             pc_o <= pc_o;
30     end
31 end
```

```
14 always@ (a or b or ci) begin
15     tmp = a + b + ci;
16 end
```
 
# always Blocks (cont.)

```
1 module clock_gen(phi1, phi2);
2
3 output phi1, phi2;
4 reg phi1, phi2;
5
6 initial begin
7     phi1 = 0; phi2 = 0;
8 end
9
10 always #100 phi1 = ~phi1;
11
12 always @(posedge phi1)
13 begin
14     phi2 = 1;
15     #50 phi2 = 0;
16     #50 phi2 = 1;
17     #50 phi2 = 0;
18 end
19
20 endmodule
```



# Procedural Assignment

- Procedural assignments drive values or expressions onto registers

```
1 module Full_Adder(sum, cout, a, b, ci);
2
3 //Interface
4 input      [31:0] a, b;
5 input      ci;
6 output     [31:0] sum;
7 output     cout;
8
9 reg        [32:0] tmp;
10 // Calculation (with Always Procedural Block)
11 assign sum = tmp[31:0];
12 assign cout = tmp[32];
13
14 always@ (a or b or ci) begin
15     tmp = a + b + ci;
16 end
17
18 endmodule
```

Procedural assignments



# Common mistakes

```
1 module f_adder(sum, co, a, b, ci);  
2  
3 output sum, co;  
4 input a, b, ci;  
5 reg sum_reg;  
6  
7 sum_reg = a ^ b ^ ci;  
8  
9 always @(a or b or ci)  
10     assign co = (a&b) | (b&ci) | (ci&a);  
11  
12 endmodule
```

A procedural assignment **must** be inside procedural blocks


A continuous assignment statement **cannot** be inside procedural blocks


 
# Blocking and Non-blocking Procedural Assignment


- Blocking procedural assignment

```
always @(posedge clock) begin
    x = a;
    y = x;
    z = y;
end
```



- Non-blocking procedural assignment
 
```
always @(posedge clock) begin
    x <= a;
    y <= x;
    z <= y;
end
```



# Conditional Statements

- if and if-else statement

```
if (expression)
    statement
```

```
if (expression)
    statement
else
    statement
```

```
if (expression)
    statement
else if (expression)
    statement
else
    statement
```

```
if (rega >= regb)
    result = 1;
else
    result = 0;
```

Ex1

```
if (index > 0)
    if (rega > regb)
        result = rega;
    else
        result = 0;
else
    $display("[WARNING] index is equal or smaller than 0!")
```

Ex2

# Conditional Statements

- case statement



```
10 `define AND 3'b000
11 `define OR 3'b001
12 `define ADD 3'b010
13 `define SUB 3'b110
14 `define SLT 3'b111
15 `define MUL 3'b011
16
17 always @ (data1_i or data2_i or ALUCtrl_i)
18 begin
19     case (ALUCtrl_i)
20         `AND: data_reg = data1_i & data2_i;
21         `OR: data_reg = data1_i | data2_i;
22         `ADD: data_reg = data1_i + data2_i;
23         `SUB: data_reg = data1_i - data2_i;
24         `SLT: data_reg = (data1_i < data2_i)? 1 : 0;
25         `MUL: data_reg = data1_i * data2_i;
26     endcase
27 end
```

# Outline

- Introduction
- Major Data Types
- Operations
- Behavior Modeling
- **Structure Modeling**

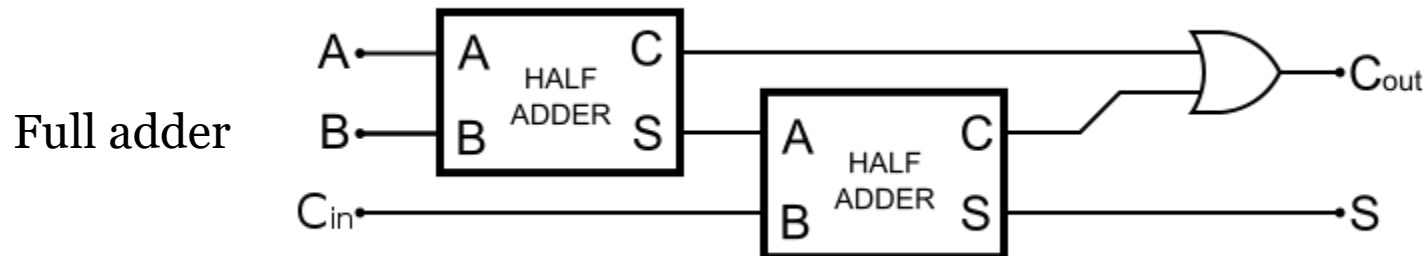 
# Structure Modeling

- Connecting components with each other to create a more complex component




# Structure Modeling

Half adder

 

Full adder

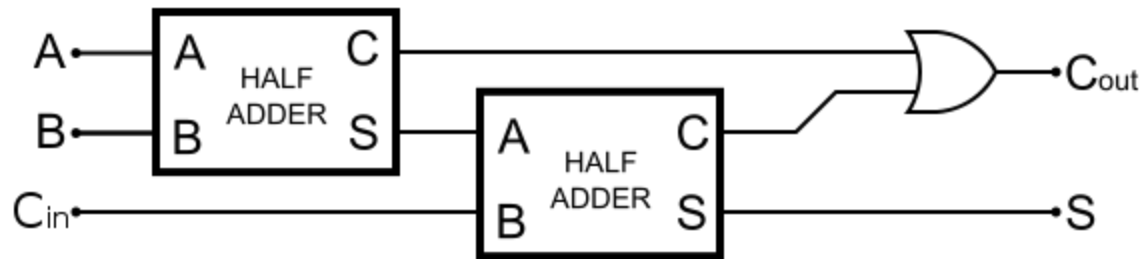

```
1 module HA(a, b, sum, co);
2
3 input a, b;
4 output sum, co;
5
6 assign sum = a ^ b;
7 assign co = a & b;
8
9 endmodule
```

```
1 module FA(A, B, cin, sum, cout);
2
3 input A, B, cin;
4 output sum, cout;
5
6 wire sum0, co0, col;
7
8 HA ha0(A, B, sum0, co0);
9 HA ha1(sum0, cin, sum, col);
10
11 assign cout = co0 ^ col;
12
13 endmodule
```